

# Group 10 RISC V

Mohamed Mahmoud Elfeki	Verification
Ehab Mostafa Farghly	Design

# Top level architecture of RISC V with cache memory

412

CHAPTER SEVEN Microarchitecture


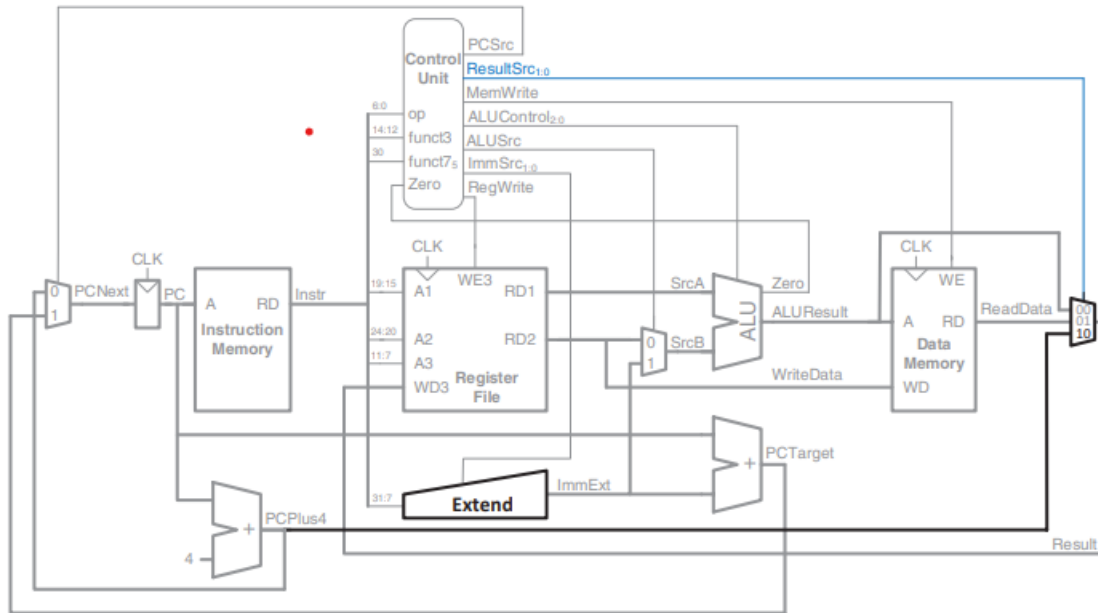


Figure 7.15 Enhanced datapath for `jal`


The main difference between this architecture and the architecture with cache memory that data memory has 2 more signals `stall` and `memory read stall` signal is output from this block and input to the PC if its value equal 1 it will stall PC and prevent it from incrementing and the signal `memory read` will come from control unit and gives value 1 only when the opcode is `LW` Instruction

# Top level architecture of cache memory

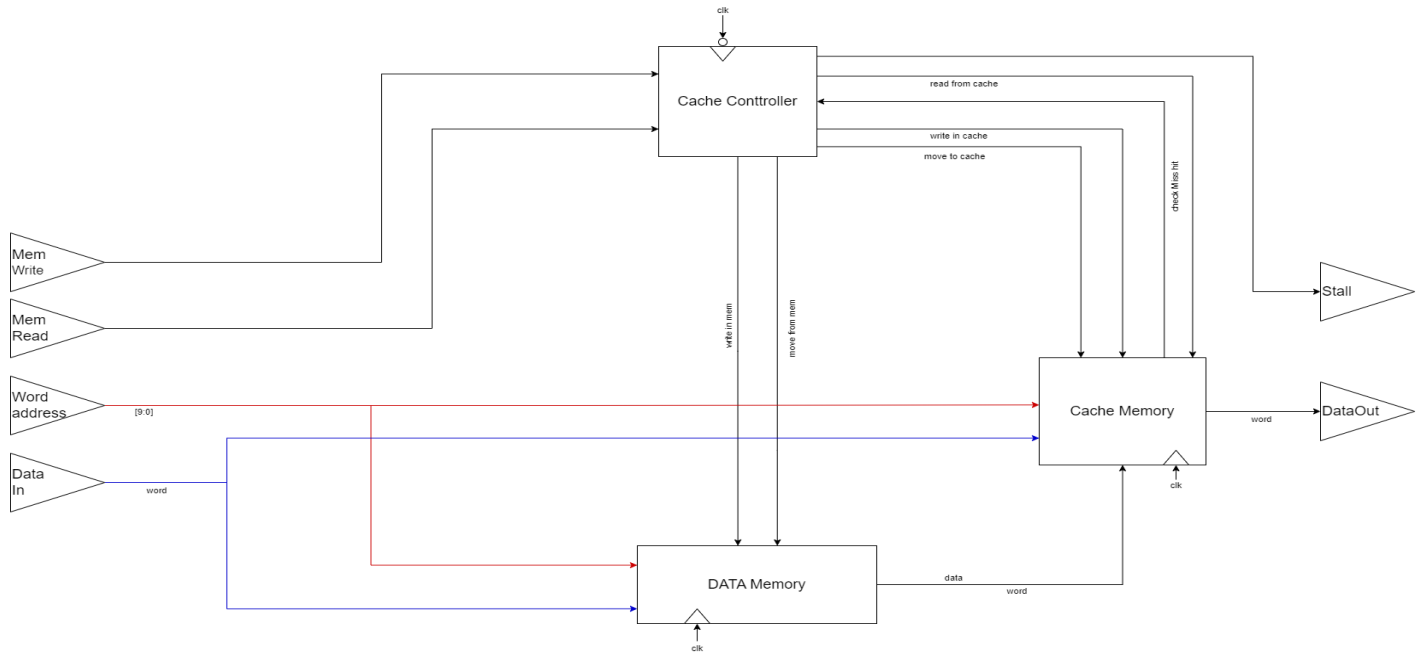

This is the block diagram representing our implementation the cache controller works at the negative edge of clk that come from RISC V

# FSM

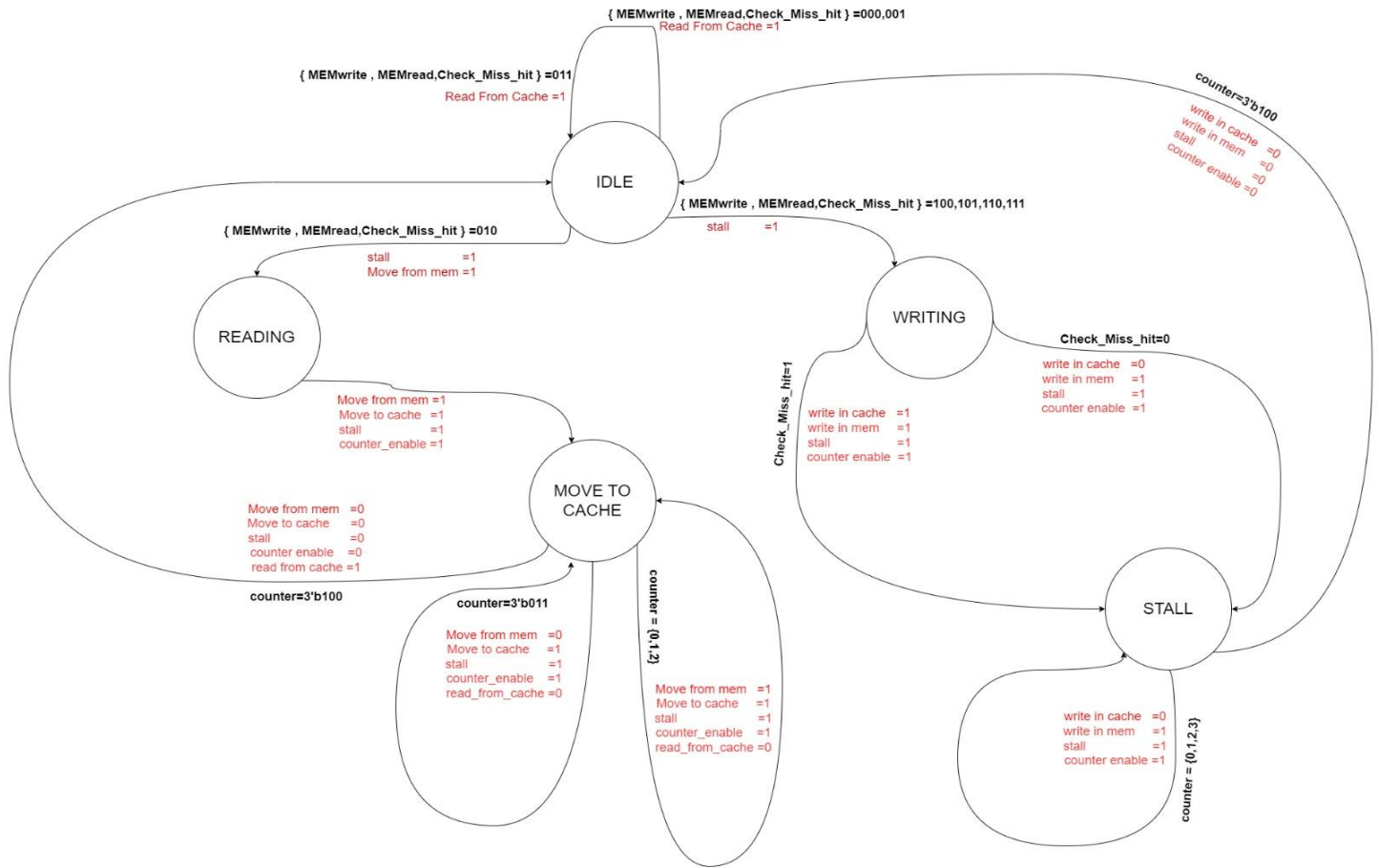

## Code of blocks

```
module cache_controller(  
    input wire      clk,rst,  
    input wire      Mem_Write,Mem_Read,  
    input wire      check_Miss_hit,  
  
    output reg       write_in_mem,  
    output reg       write_in_cache,  
    output reg       move_from_mem,  
    output reg       move_to_cache,  
    output reg       read_from_cache,  
    output reg       stall  
);  
parameter IDLE      =3'b000,  
          READING    =3'b001,  
          MOVE_TO_CACHE =3'b010,  
          WRITING     =3'b011,  
          STALL       =3'b100;  
  
reg [2:0] current_state,next_state;  
reg [2:0] counter;  
reg      counter_enable;  
  
always @(negedge clk or negedge rst)  
    begin  
        if(!rst)  
            begin  
                counter <='b0;  
            end  
        else if (counter_enable)  
            begin  
                counter <= counter +'b1;  
            end  
        else  
            begin  
                counter <= 'b0;  
            end  
    end  
  
always @(negedge clk or negedge rst)  
    begin  
        if(!rst)  
            begin  
                current_state <=IDLE;
```

```

        end
    else
        begin
            current_state <= next_state;
        end
    end
end

always@(*)
begin
    write_in_mem      ='b0;
    write_in_cache    ='b0;
    move_from_mem     ='b0;
    move_to_cache     ='b0;
    read_from_cache   ='b0;
    counter_enable    ='b0;

    case(current_state)
        IDLE          : begin
            if((Mem_Read=='b1) && (Mem_Write == 'b0) && (check_Miss_hit=='b1)
)
                begin
                    next_state = IDLE;
                    stall      ='b0;
                    read_from_cache='b1;
                end

            else if((Mem_Read=='b1) && (Mem_Write == 'b0) &&
(check_Miss_hit=='b0) )
                begin
                    next_state = READING;
                    stall='b1;
                    move_from_mem = 'b1;

                end

            else if((Mem_Read=='b0) && (Mem_Write == 'b1) )
                begin
                    next_state = WRITING;
                    stall='b1;

                end

            else
                begin
                    next_state =IDLE;
                    stall='b0;

                end

            end

        end

        READING      : begin

```

```

        next_state      = MOVE_TO_CACHE;
        move_from_mem   = 'b1;
        move_to_cache   = 'b1;
        stall           = 'b1;  /***/
        counter_enable  = 'b1;

    end

MOVE_TO_CACHE : begin

    if(counter == 3'b100)
        begin
            next_state      = IDLE;
            read_from_cache = 'b1;
            stall           = 'b0;
            counter_enable  = 'b0;
            move_from_mem   = 'b0;
            move_to_cache   = 'b0;
        end
    else if(counter == 3'b011)
        begin
            next_state      = MOVE_TO_CACHE;
            read_from_cache = 'b0;
            stall           = 'b1;
            counter_enable  = 'b1;
            move_from_mem   = 'b0;
            move_to_cache   = 'b1;
        end
    else
        begin
            next_state      = MOVE_TO_CACHE;
            move_from_mem   = 'b1;
            move_to_cache   = 'b1;
            stall           = 'b1;
            counter_enable  = 'b1;
        end
    end

WRITING : begin
    counter_enable='b1;

    if(check_Miss_hit )    // 1 hit      0 Miss
        begin
            write_in_cache = 'b1;
            write_in_mem   = 'b1;
            stall           = 'b1;
            next_state      =STALL;
        end
    else
        begin
            write_in_cache = 'b0;

```

```

        write_in_mem    ='b1;
        stall           ='b1;
        next_state      =STALL;
    end
end

STALL      : begin
    counter_enable    ='b1;

    if(counter == 'b100)
        begin
            stall='b0;
            write_in_cache='b0;
            write_in_mem='b0;
            next_state =IDLE;
            counter_enable  ='b0;
        end
    else
        begin
            stall='b1;
            write_in_cache='b0;
            write_in_mem='b1;
            next_state =STALL;
            counter_enable  ='b1;
        end
    end

default    : begin
    write_in_mem    ='b0;
    write_in_cache  ='b0;
    move_from_mem   ='b0;
    read_from_cache ='b0;
    stall           ='b0;
    counter_enable  ='b0;
    next_state      =IDLE;
end

endcase
end
endmodule

```



```

module cache_Memory (
    input    wire      clk,rst,
    input    wire  [9:0] Word_address,
    input    wire  [31:0] data,
    input    wire  [31:0] Data_IN,
    input    wire      write_in_cache,read_from_cache,
    input    wire      move_to_cache,

    output   reg      check_Miss_hit,
    output   reg  [31:0] Data_Out
);

reg [31:0]  cache_mem [0:127];
reg [3:0]   valid_tag [0:31];
reg [1:0]   move_count;
integer i,k;

always @(posedge clk or negedge rst )
begin
    if(!rst)
        begin
            for (i=0;i<128;i=i+1)
                begin
                    cache_mem[i]<='b0;
                end
            for (k=0;k<32;k=k+1)
                begin
                    valid_tag[k]<='b0;
                end
            move_count <= 'b0;
        end

    else if (write_in_cache)
        begin
            cache_mem [Word_address[6:0]] <= Data_IN;
            valid_tag [Word_address[6:2]] <={1'b1,Word_address[9:7]};
        end

    else if (move_to_cache)
        begin
            cache_mem [{Word_address[6:2],move_count}] <= data;
            valid_tag [Word_address[6:2]] <={1'b1,Word_address[9:7]};
            move_count <= move_count +'b1;
        end

end

always @(*)

```

```

begin
    if (valid_tag[Word_address[6:2]] == {1'b1 , Word_address [9:7]})
        begin
            check_Miss_hit ='b1;
        end
    else
        begin
            check_Miss_hit ='b0;
        end
    end
end
always @(*) begin
    if (!rst) begin
        Data_Out='b0;

    end
    else if (read_from_cache)
        begin
            Data_Out = cache_mem [Word_address[6:0]];
        end
    else begin
        Data_Out='b0;
    end
end

end
endmodule

```

```

module data_memory (
    input      wire      clk,rst,
    input      wire      [9:0] Word_address,
    input      wire      [31:0] Data_In,
    input      wire      write_in_mem,
    input      wire      move_to_cache,

    output      reg      [31:0]      data
);

    reg [31:0]  main_memory [0:1023];
    reg [1:0]   address_count;
    integer     i;

always@(posedge clk or negedge rst)
    begin
        if(!rst)
            begin
                for(i=0;i<1024;i=i+1)
                    main_memory[i] <='b0;
                    address_count <='b0;
                    data <='b0;
                end
            else
                begin
                    if(write_in_mem)
                        begin
                            main_memory[Word_address] <= Data_In;
                            address_count <='b0;
                        end
                    else if (move_to_cache)
                        begin
                            address_count <=address_count+1;
                            data <= main_memory[{Word_address[9:2],address_count}];
                        end
                    else
                        begin
                            address_count <='b0;
                        end
                end
            end
    end

endmodule

```

```

module cache_Memory_top (
    input  wire      clk,rst,
    input  wire      Mem_Write,Mem_Read,
    input  wire [9:0] Word_address,
    input  wire [31:0] Data_In,

    output wire      stall,
    output wire [31:0] Data_Out
);

```

```

/*****/

```

```

wire      check_Miss_hit;
wire      write_in_mem,write_in_cache;
wire      move_from_mem;
wire      move_to_cache;
wire      read_from_cache;

```

```

cache_controller u0(
    .clk(clk),
    .rst(rst),
    .Mem_Write(Mem_Write),
    .Mem_Read(Mem_Read),
    .check_Miss_hit(check_Miss_hit),

    .write_in_mem(write_in_mem),
    .write_in_cache(write_in_cache),
    .move_from_mem(move_from_mem),
    .move_to_cache(move_to_cache),
    .read_from_cache(read_from_cache),
    .stall(stall)
);

```

```

/*****/

```

```

wire [31:0]      data;

```

```

cache_Memory u1(
    .clk(clk),
    .rst(rst),
    .Word_address(Word_address),
    .data(data),
    .Data_IN(Data_In),
    .write_in_cache(write_in_cache),
    .read_from_cache(read_from_cache),
    .move_to_cache(move_to_cache),

    .check_Miss_hit(check_Miss_hit),
    .Data_Out(Data_Out)
);

```

```

/*****/

```

```
data_memory u2(  
    .clk(clk),  
    .rst(rst),  
    .Word_address(Word_address),  
    .Data_In(Data_In),  
    .write_in_mem(write_in_mem),  
    .move_to_cache(move_from_mem),  
  
    .data(data)  
);  
  
endmodule
```

# Test cases for design and simulation result of design

## Test cases for cache memory before integration

```
/* ***** testcases ***** */
****/

/* scenario writing in block and check the reading operations of them miss first then
all hit */
/** write operations **/

write_data('b111_00010_01','d16 ');
write_data('b111_00010_10','d8 ');
write_data('b111_00010_00','d4 ');
write_data('b111_00010_11','d2 ');

/** read operations **/

read_data ('b111_00010_11);
read_data ('b111_00010_10);
read_data ('b111_00010_01);
read_data ('b111_00010_00);

/* scenario writing in block exist in cache and check the writing operations of them
hit and store in cache and memory in same time */
/** write operations **/

write_data('b111_00010_01','d100 ');
write_data('b111_00010_10','d120 ');

/** read operations **/

read_data ('b111_00010_00);
read_data ('b111_00010_01);
read_data ('b111_00010_10);
read_data ('b111_00010_11);

/* scenario addressing same block different in tag with different values */
/** write operations **/

write_data('b101_00010_01','d200 ');
write_data('b101_00010_10','d220 ');

/** read operations **/

read_data ('b101_00010_00);
read_data ('b101_00010_01);
```

```

read_data ('b101_00010_10);
read_data ('b111_00010_11);
read_data ('b111_00010_01);

/***** Random processes *****/
/** write operations **/

write_data('b000_00110_01 ','d60 '); // Block 6 tag =0 ofsset=1
write_data('b011_01010_01 ','d100 '); // Block 10 tag =3 offset=1
write_data('b010_00111_01 ','d20 '); // Block 2 tag=2 offset=1
write_data('b110_10010_10 ','d60 '); // Blcok
18 tag=6 offset=2 /***/
write_data('b000_01011_00 ','d110 '); // Block 11 tag =0 offset=0
write_data('b101_10010_11 ','d200 '); // Block 18 tag=5 offset=3
write_data('b001_00000_11 ','d1000); // Block 0 tag =1 offset=3
write_data('b001_10011_01 ','d190 '); // Block 19 tag =1 offset=1
write_data('b111_11010_10 ','d260 '); // Block 26 tag =7 offset=2

/** read operations **/



read_data ('b000_00110_01);
read_data ('b011_01010_01);
read_data ('b010_00111_01);
read_data ('b110_10010_10);
read_data ('b110_10010_10);
read_data ('b000_01011_00);
read_data ('b101_10010_11);
read_data ('b001_00000_11);
read_data ('b001_10011_01);
read_data ('b111_11010_10);

```


The timing diagram displays the following signals and their values over time:

Signal	Width	Value
clk	1b0	1
rst	1b1	0
Mem_Write	1b0	0
Mem_Read	1b0	0
Word_address	10b	1110001011
Data_In	32'd2	2
stall	1b0	0
Data_Out	32'd0	0

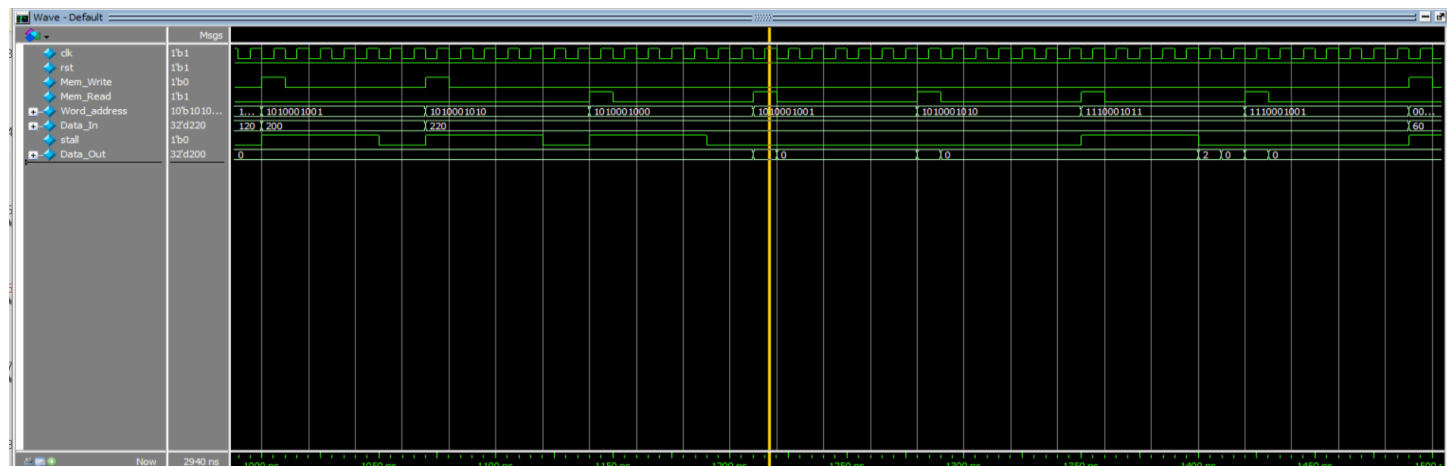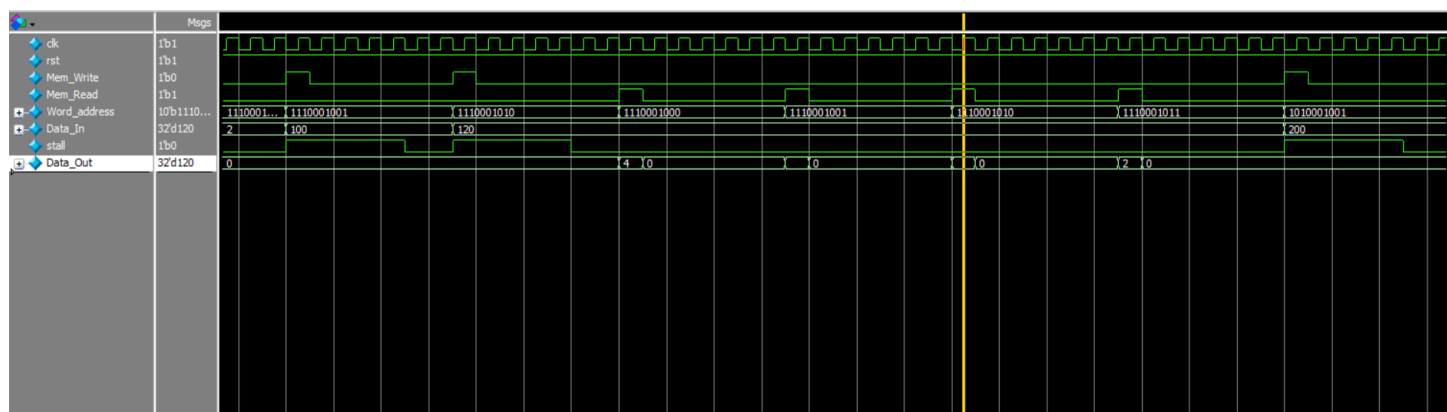The waveform view shows a clock signal (clk) and a reset signal (rst). The memory write (Mem\_Write) and read (Mem\_Read) signals are both low. The word address (Word\_address) is 1110001011. The data in (Data\_In) is 2. The stall signal is low. The data out (Data\_Out) is 0. A cursor is positioned at 292 ns.





 


**Test cases for cache memory and RISC after integration**


```

00F00093      //addi x1 x0 15
01400113      //addi x2 x0 20
01900193      //addi x3 x0 25
01E00213      //addi x4 x0 30
01900293      //addi x5 x0 25
0020A2A3      //sw x2 5(x1)
0030A323      //sw x3 6(x1)
0040A3A3      //sw x4 7(x1)
0050A423      //sw x5 8(x1)
0050A303      //lw x6 5(x1)
0060A383      //lw x7 6(x1)
0070A403      //lw x8 7(x1)
0080A483      //lw x9 8(x1)

```

**Simulation result in this case**

 

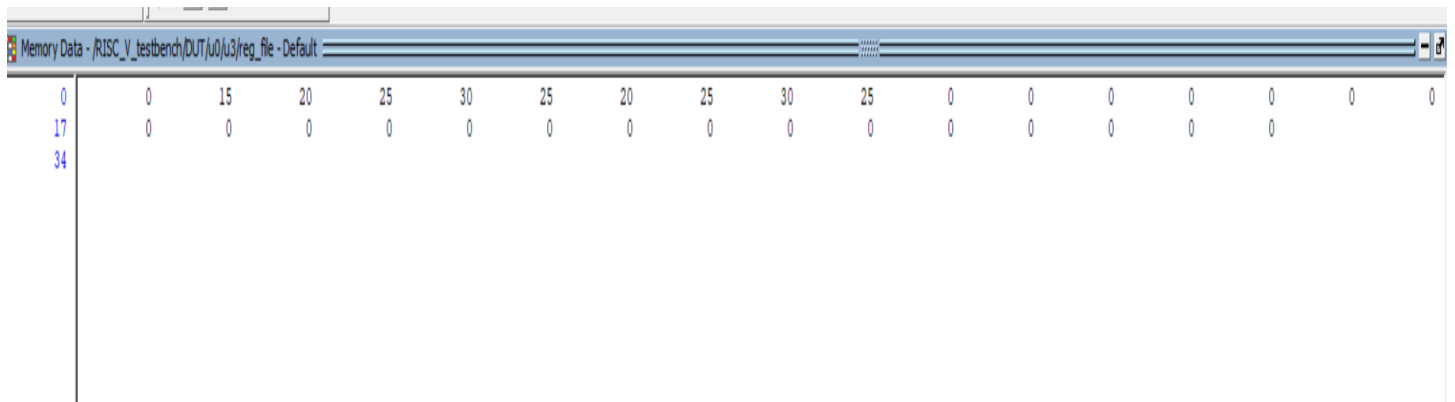

As we see in wave form stall signal is high five times as miss occur in all 4 times of storing and miss occur in first time of loading then hit occur and register files contain the proper results